

期中
國立陽明交通大學 學期 考試答案紙

National Yang Ming Chiao Tung University Midterm/Final Examination Answer Sheet

記分
Score
94

112 學年度第 1 學期
Semester of Year


科目 VLSI 系所 電機 年級 3
Course title Department Year

考試日期 112 年 11 月 13 日 學號 110511118 姓名 陳孟頌
Date Y M D Student ID no. Name



從此處開始寫起 Please write from here

- A. 1. ~~F~~ 2. F 3. T 4. F 5. F
6. F 7. F 8. T 9. T 10. T

B.

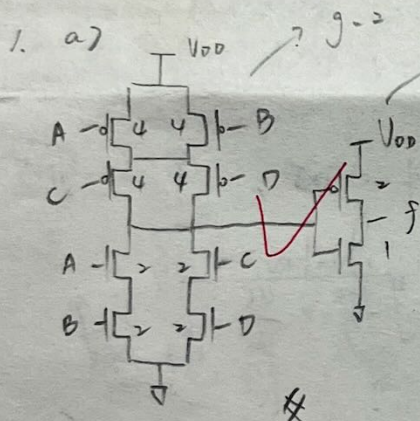

  
$G = 2 \quad B = 1 \quad P = 4 + 1 = 5$
 $\hat{f} = \sqrt[3]{GBH} = \sqrt[3]{2H}$
 $D = 2 \cdot \sqrt[3]{2H} + 5$



$G = \frac{4}{3} \times \frac{4}{3} = \frac{16}{9} \quad B = 1 \quad P = 2 + 2 = 4$
 $\hat{f} = \sqrt[3]{\frac{16}{9}H} = \frac{4}{3}\sqrt[3]{H}$
 $D = 2 \cdot \frac{4}{3}\sqrt[3]{H} + 4 = \frac{8}{3}\sqrt[3]{H} + 4$

1. For more transistors
 explain: 2. MOS are voltage-controlled devices
 4. Noise will change behavior in dynamic circuit.
 5. Pseudo-NMOS doesn't have better performance in power consumption
 6. Area is bigger
 7. g can be less than 1

c)

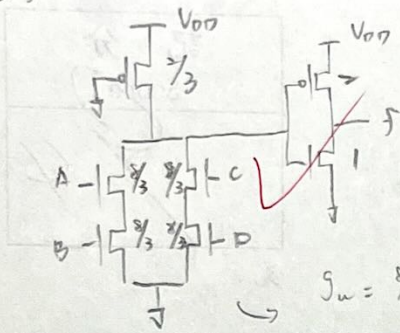

Requirement: ① connect the remaining pMOS to GND
② make pMOS about $\frac{1}{4}$ effective strength of pull-down network.



$$g_u = \frac{1}{3}, g_d = \frac{1}{9}, g_{avg} = \frac{1}{9}$$

$$P_u = 6, P_d = 2, P_{avg} = 4$$

$$\Rightarrow D = 2 \cdot \sqrt{\frac{16}{9}} H + 4$$

$$= \frac{8}{3} \sqrt{H} + 4$$

→ speed is better than (a)

  

	NAND3	NOR2
g	$\frac{5}{3}$	$\frac{5}{3}$
P	3	2

$$b) G = \frac{4}{3} \times \frac{5}{3} \times \frac{5}{3} = \frac{100}{27}$$

$$\Rightarrow F = GBH = 125, \hat{f} = \sqrt[3]{125} = 5$$

$$H = \frac{45}{8}$$

$$\Rightarrow D = 3 \cdot \sqrt[3]{\frac{100}{27} \times \frac{45}{8} \times 6} + 7$$


$$B = 2 \times 3 = 6$$

$$P = 2 + 3 + 2 = 7$$


$$= 3 \times 5 + 7 = 22$$

c)
 
$$g = \frac{45}{5} \times \frac{5}{3} = 15 \rightarrow$$



 
$$x = \frac{15 \times 2}{5} \times \frac{5}{3} = 10 \rightarrow$$





2) No, if we only down-size the top 2-3 inputs, some path are faster than the others, and we still have to wait for the latest path.

3. a)

 


b)

  

⇒ 若 well contacts 沒有做好，會導致電晶體內部偏壓跑掉，會在各材料交界處形成順向偏壓，使大電流通過，造成電晶體乃至電路燒掉或無法正常工作 → latch-up #

4. a)

 

$$P_u = \frac{2}{3} + \frac{4}{3}k$$

$$P_d = \frac{2}{3} + \frac{4}{3}k$$

$$P_{avg} = \frac{4}{9} + \frac{8}{9}k$$

$$G = 1 \times \frac{8}{9} = \frac{8}{9}$$


$$B = 1$$

$$H = \frac{H}{1} = H$$

$$P = 1 + \frac{4}{9} + \frac{8}{9}k = \frac{13}{9} + \frac{8}{9}k$$

$$\Rightarrow F = \frac{8}{9}H, \hat{f} = \frac{2}{3}\sqrt{2H}$$
 
$$D = 2 \cdot \frac{2}{3}\sqrt{2H} + \frac{13}{9} + \frac{8}{9}k$$



calculate delay of the stage = $\frac{3}{4}R \left(\frac{4}{3}C + \frac{C}{2} \right) + \left(\frac{3}{4}R + R \right) \left(\frac{C}{2} + H \right)$

= $\frac{11}{8}RC + \frac{7}{8}RC + \frac{7}{4}RH$

= $\frac{18}{8}RC + \frac{7}{4}RH$

= $\frac{9}{4}RC + \frac{7}{4}RH$ #